

CPE 462


VHDL: Simulation and Synthesis

Topic #08 - a) Components

COMPONENT

- A COMPONENT is simply a piece of conventional code
- Conventional code = LIBRARY declarations + ENTITY + ARCHITECTURE
- However, by declaring such code as being a COMPONENT, it can then be used within another circuit, thus allowing the construction of hierarchical designs.
- A COMPONENT is also another way of partitioning a code and providing code sharing and code reuse.
- For example, commonly used circuits (FF, multipliers, adders,...) can be placed in a LIBRARY, so any project can make use of them without having to explicitly rewrite such codes.


Motivational example

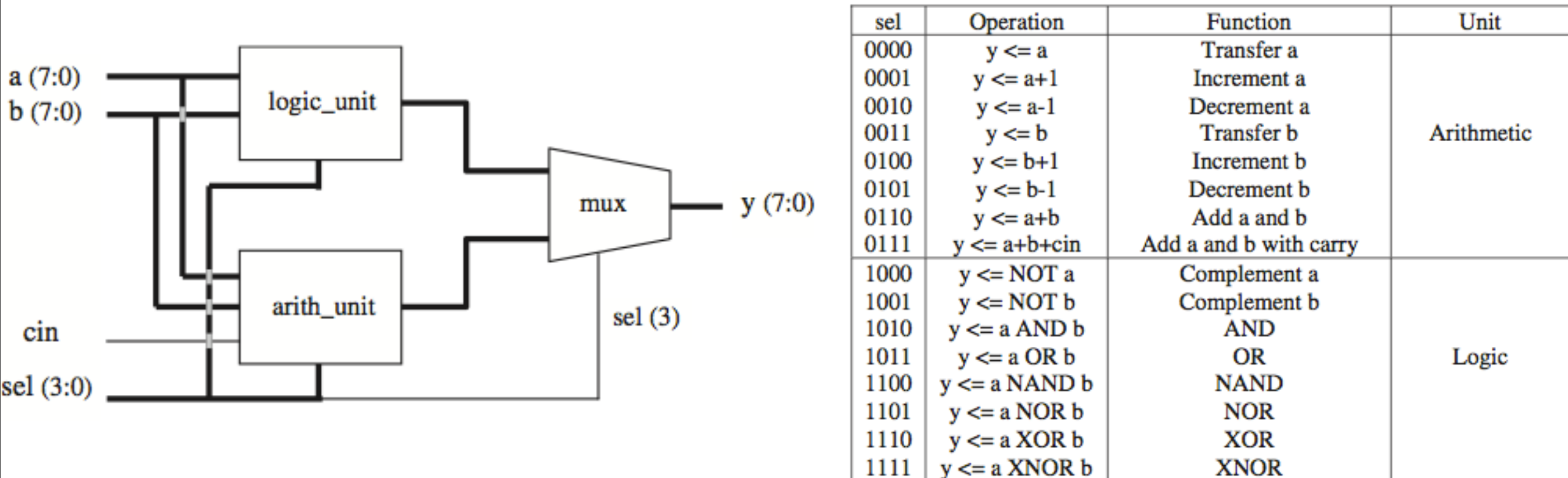

- Instead of writing the entire code in a single VHDL architecture, I divide my design into blocks.
- Each block is a component and we can re-use components!
- Becomes much easier to collaborate in teams, if design is modular.

Let's build a modular design from scratch

AOI Gate

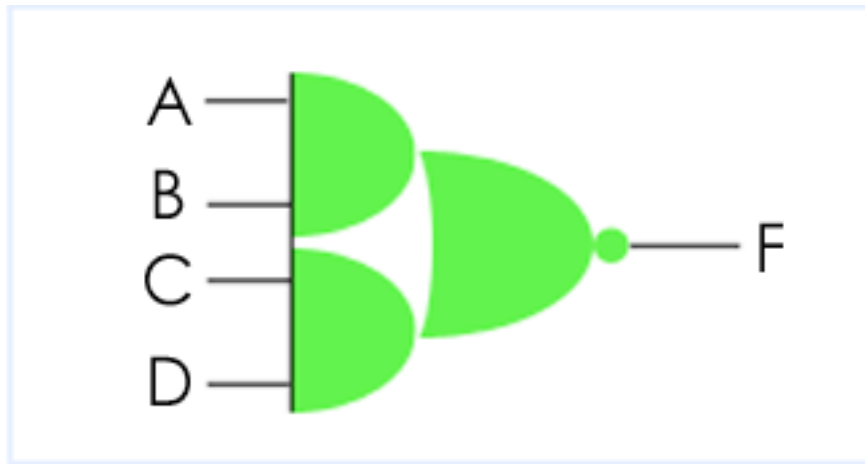


$$F = \overline{(A \wedge B) \vee (C \wedge D)}$$

2-2 AOI				
INPUT				OUTPUT
A	B	C	D	F
0	X	X	0	1
X	0	X	0	1
0	X	0	X	1
X	0	0	X	1
1	1	X	X	0
X	X	1	1	0

- We want to describe an and-or-invert (AOI) gate in VHDL.
- If we consider the AOI gate as a single chip package, it will have four input pins and one output pin
- AOI gate is particularly popular because in CMOS technology it can be implemented as a single gate, whose size is less than if the AND, NOT, and OR functions were implemented separately.

AOI Gate

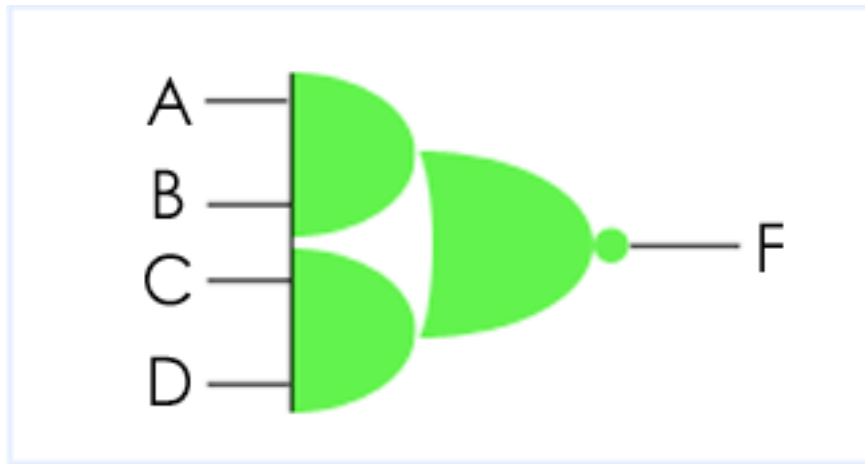

$$F = \overline{(A \wedge B) \vee (C \wedge D)}$$

2-2 AOI				
INPUT				OUTPUT
A	B	C	D	F
0	X	X	0	1
X	0	X	0	1
0	X	0	X	1
X	0	0	X	1
1	1	X	X	0
X	X	1	1	0

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;
```

```
entity AOI is
```

```
port (
```

```
    A, B, C, D: in STD_LOGIC;
```

```
    F : out STD_LOGIC
```

```
);
```

```
end entity;
```

```
architecture V1 of AOI is
```


```
begin
```

```
    F <= not ((A and B) or (C and D));
```

```
end architecture;
```


How to implement a bigger design?

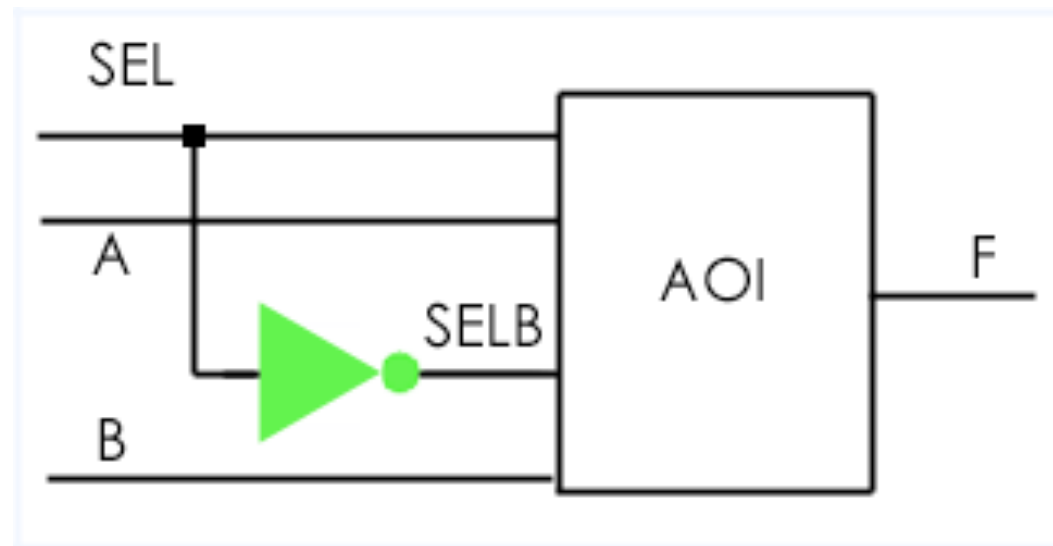- Now I want to use that AOI gate in my design.
- In particular, I want to implement the following circuit:




- Where the **INVERTER** and the **AOI** are two components inside another design.
- First I need to **instantiate** the components and **port map** them afterwards.

Instantiation

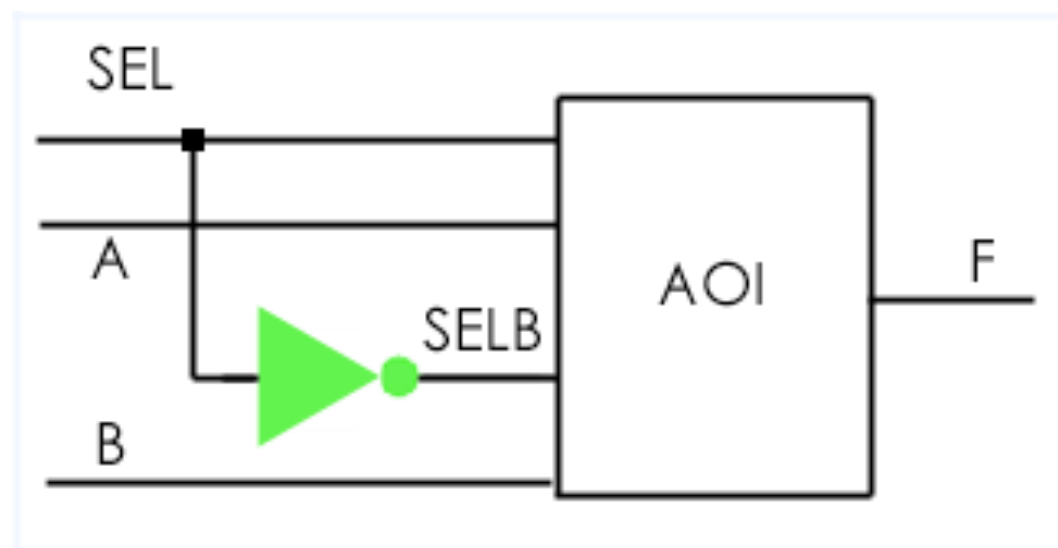

- I want to place two components inside another higher level design.
- AOI is a component.
- INVERTER is another component.
- Instantiating components, means we are inserting them into a bigger design.

Port Mapping

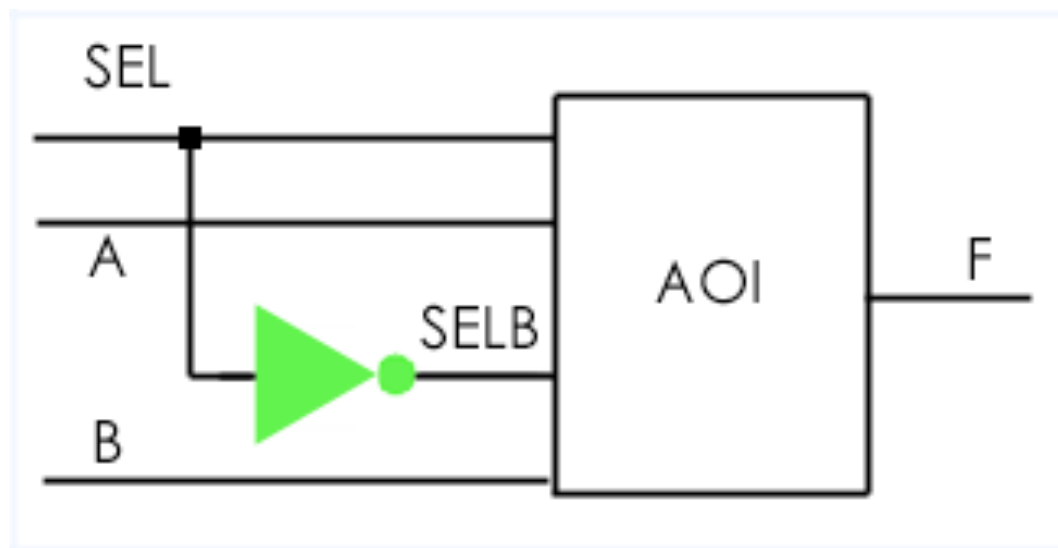

- Port Mapping means we are connecting the components to each other and to the input and output ports of the higher level design.

How to use components in VHDL

Step #1 - Create a separate VHDL file for each different component:

--inverter.vhd

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;
```

```
entity INVERTER is  
port (  
    A : in STD_LOGIC;  
    F : out STD_LOGIC  
);  
end entity;
```

```
architecture V1 of INVERTER is  
begin  
    F <= not (A);  
end architecture;
```


--aoi.vhd

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;
```

```
entity AOI is  
port (  
    A, B, C, D: in STD_LOGIC;  
    F : out STD_LOGIC  
);  
end entity;
```


```
architecture V1 of AOI is  
begin  
    F <= not ((A and B) or (C and D));  
end architecture;
```

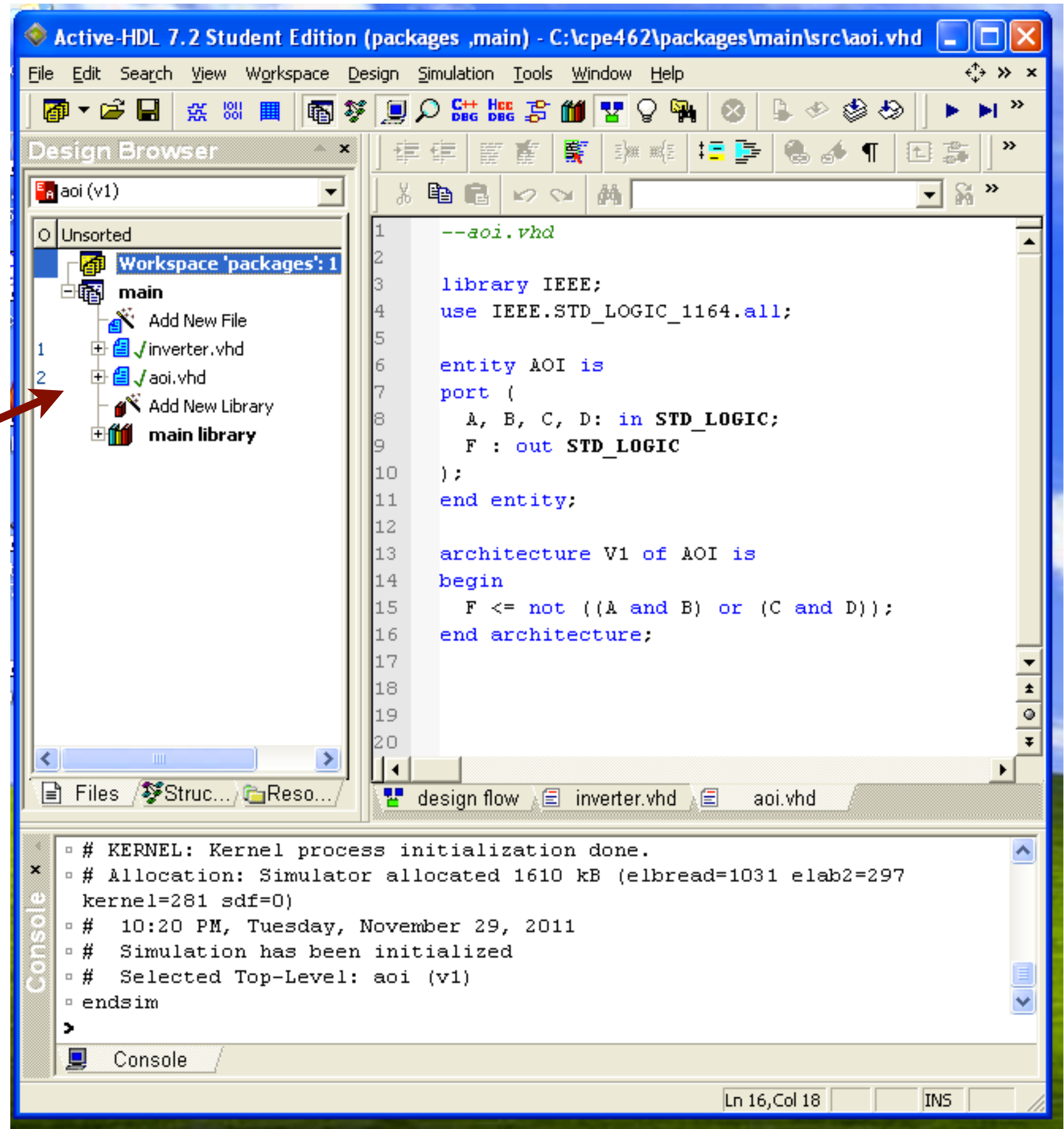Create two new files
in active HDL, and
add your code to it.



How to use components in VHDL

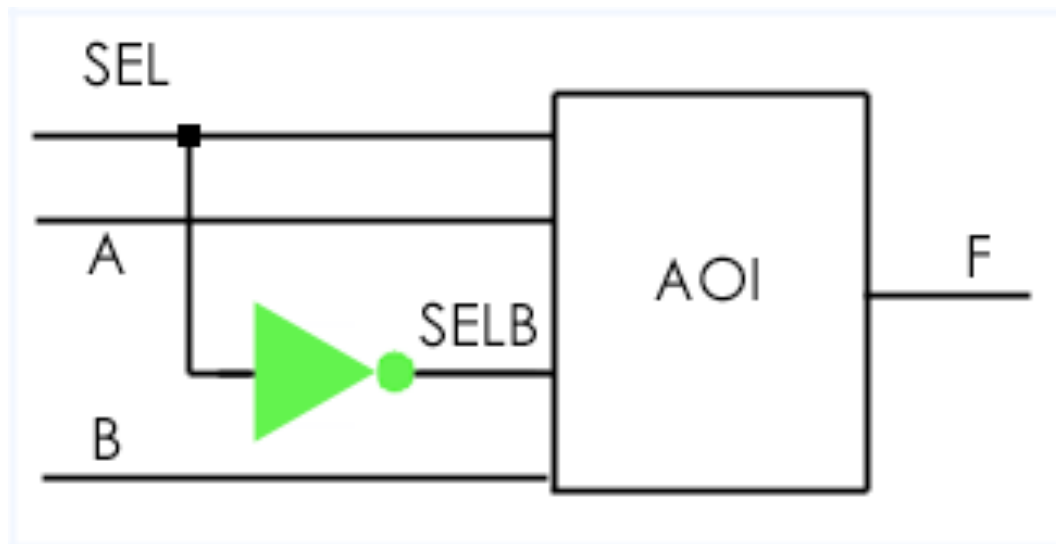Step #2 - Create another VHDL file that uses the desired components.



```
--topLevel.vhd
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;
```

```
entity topLevel is  
    port (SEL, A, B: in STD_LOGIC;  
          F : out STD_LOGIC);  
end entity;
```

```
architecture STRUCTURE of topLevel is
```



```
    component INVERTER  
        port (A: in STD_LOGIC;  
              F: out STD_LOGIC);  
    end component;
```

```
    component AOI  
        port (A, B, C, D: in STD_LOGIC;  
              F : out STD_LOGIC);  
    end component;
```



```
    signal SELB: STD_LOGIC;
```

```
begin  
    G1: INVERTER port map (SEL, SELB);  
    G2: AOI port map (SEL, A, SELB, B, F);  
end architecture;
```

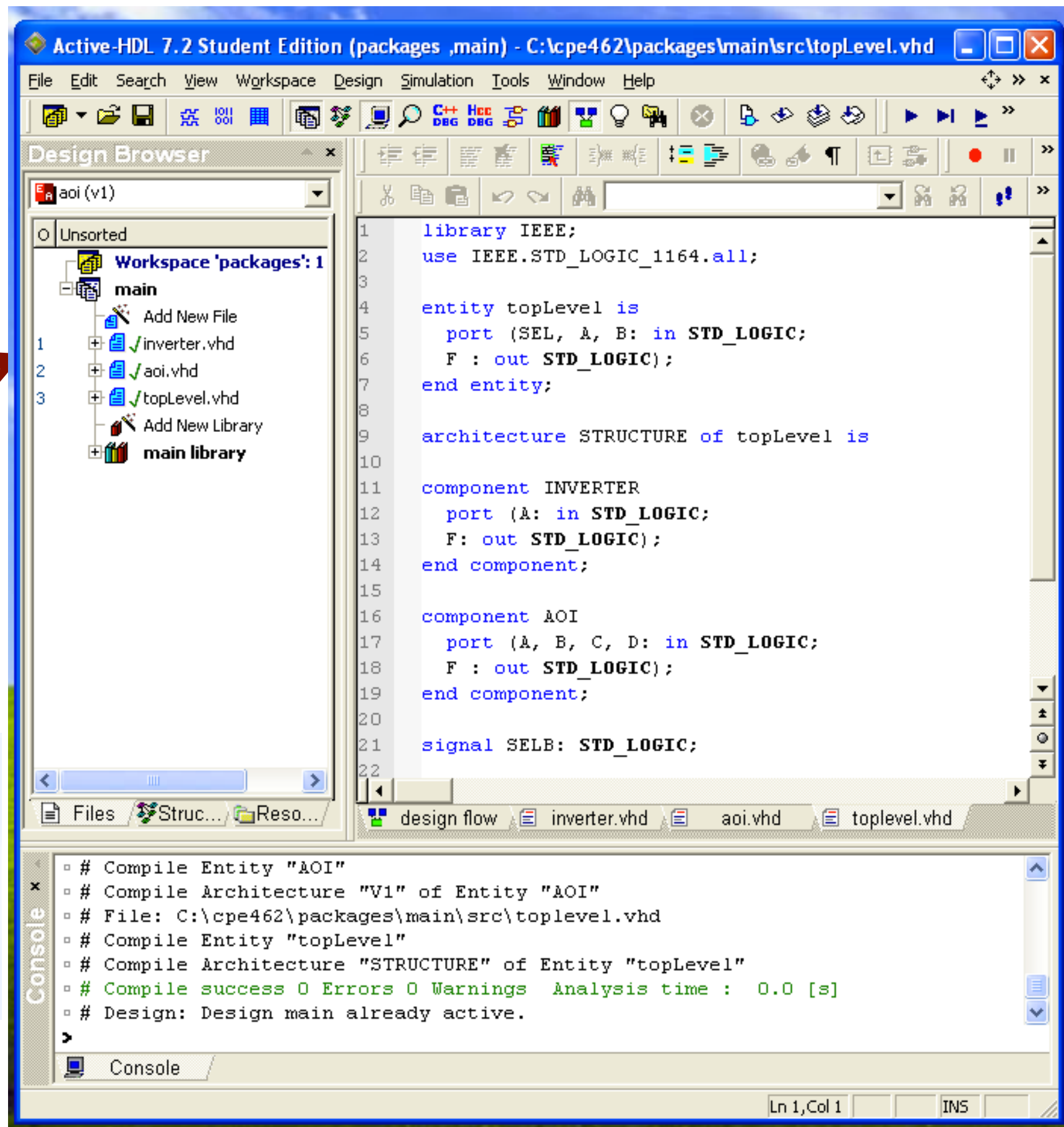
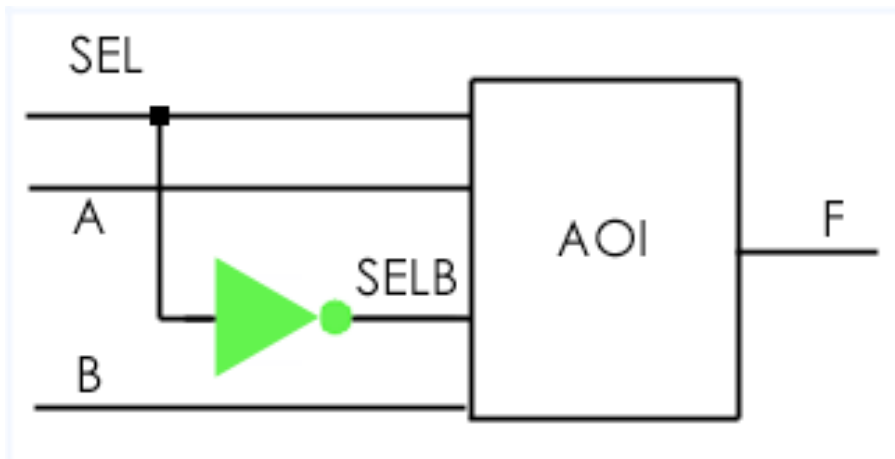
Create another file in
active HDL with the
topLevel circuit



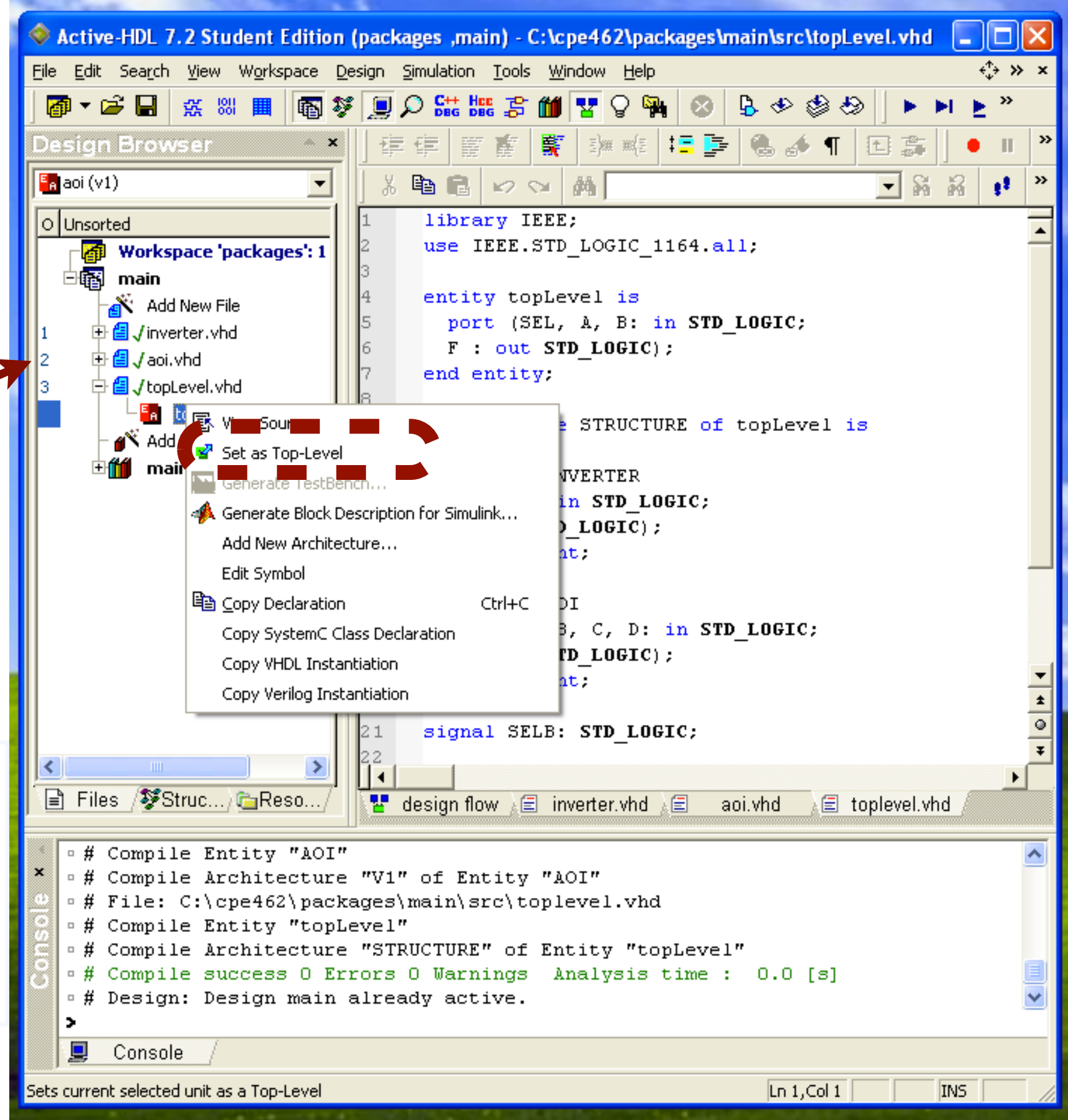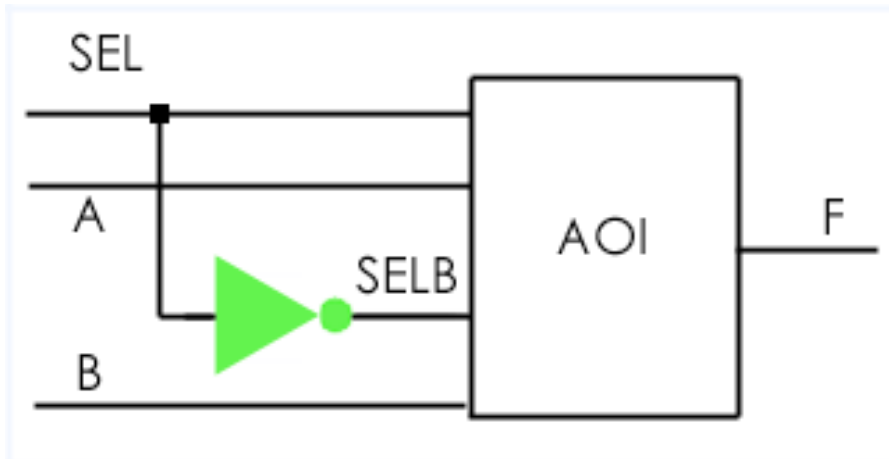Make the
topLevel.vhd file the
top level!




Simulation

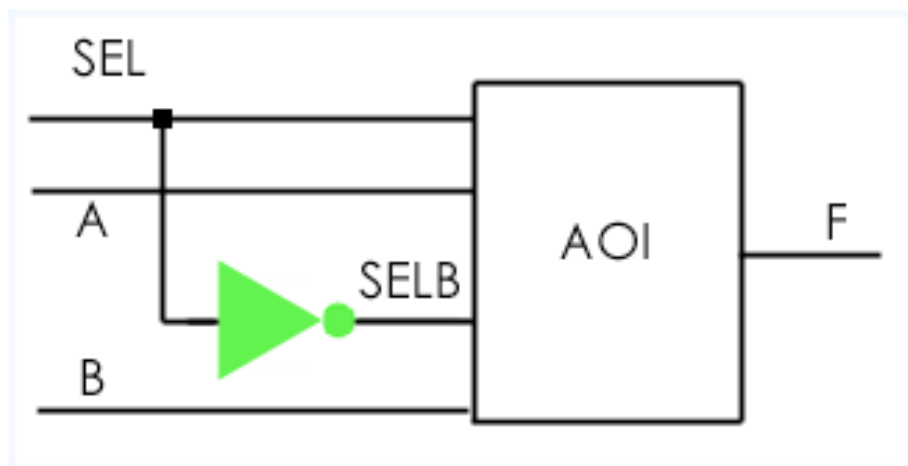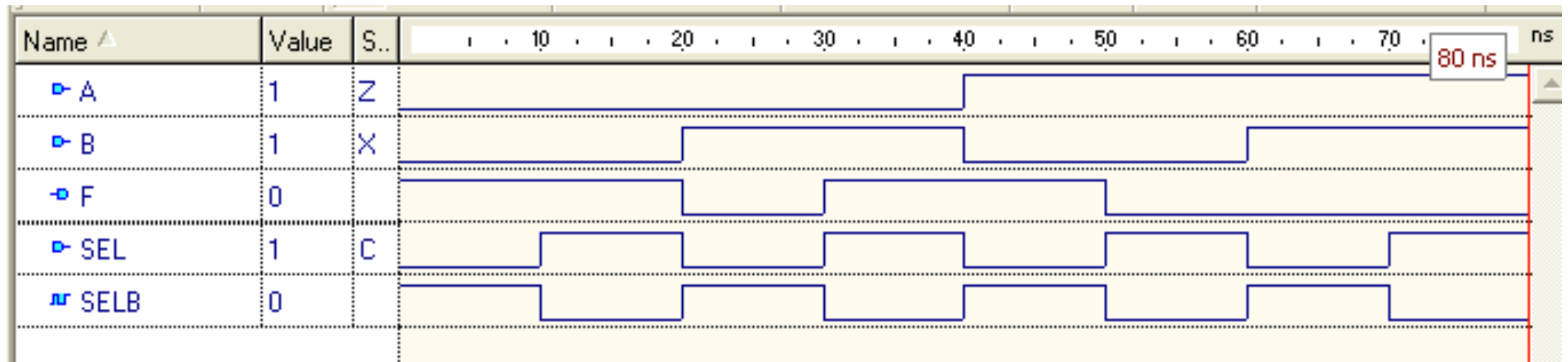

- This is an unusual 2-1 MUX
- When SEL=1, F is NOT(A)
- When SEL=0, F is NOT(B)

Detailed look at topLevel.vhd

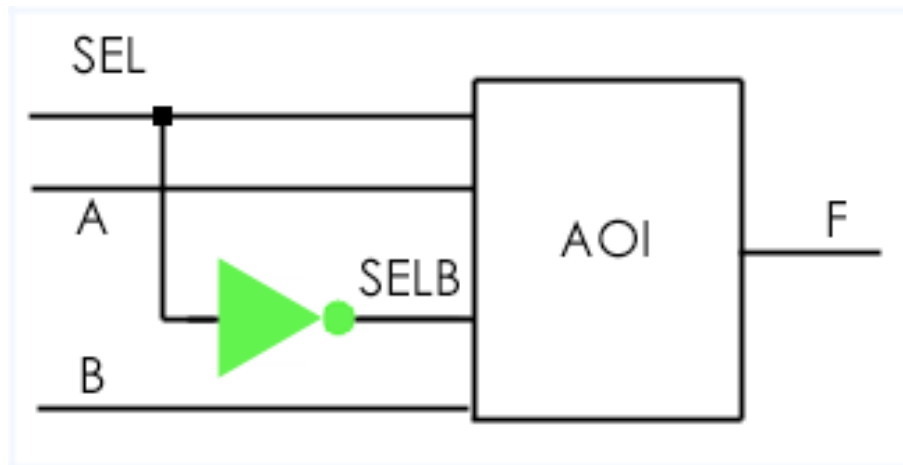- In the architecture, before the begin I must specify the components I am going to use. This is the **component declaration**.



- The component section looks very similar to the appropriate entity section.

```
--topLevel.vhd
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

```
entity topLevel is
```

```
    port (SEL, A, B: in STD_LOGIC;
```

```
          F : out STD_LOGIC);
```

```
end entity;
```

```
architecture STRUCTURE of topLevel is
```

```
    component INVERTER
```

```
        port (A: in STD_LOGIC;
```

```
              F: out STD_LOGIC);
```

```
    end component;
```

```
    component AOI
```

```
        port (A, B, C, D: in STD_LOGIC;
```

```
              F : out STD_LOGIC);
```

```
    end component;
```

```
    signal SELB: STD_LOGIC;
```

```
begin
```

```
    G1: INVERTER port map (SEL, SELB);
```

```
    G2: AOI port map (SEL, A, SELB, B, F);
```

```
end architecture;
```

topLevel.vhd

Component declaration
must be identical to the
entity part of the
respective design!

```
--aoi.vhd

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity AOI is
port (
    A, B, C, D: in STD_LOGIC;
    F : out STD_LOGIC
);
end entity;

architecture V1 of AOI is
begin
    F <= not ((A and B) or (C and D));
end architecture;
```

```
--topLevel.vhd

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity topLevel is
    port (SEL, A, B: in STD_LOGIC;
        F : out STD_LOGIC);
end entity;

architecture STRUCTURE of topLevel is

    component INVERTER
        port (A: in STD_LOGIC;
            F: out STD_LOGIC);
    end component;


    component AOI
        port (A, B, C, D: in STD_LOGIC;
            F : out STD_LOGIC);
    end component;

    signal SELB: STD_LOGIC;

begin
    G1: INVERTER port map (SEL, SELB);
    G2: AOI port map (SEL, A, SELB, B, F);
end architecture;
```

topLevel.vhd

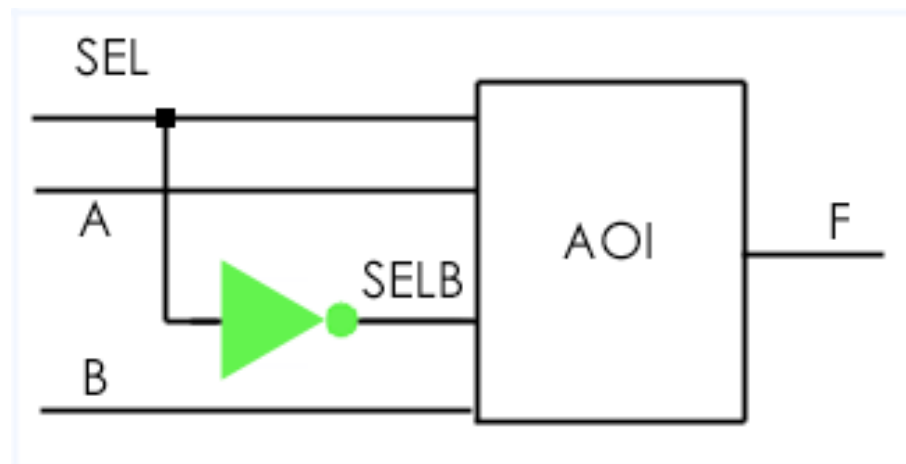- There are two instances of **INVERTER** and **AOI** through the component instantiations at the bottom of the architecture (labelled G1 and G2).
- The instance labels (G1 and G2) identify two specific instances of the components, and are mandatory.



```
--topLevel.vhd
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

```
entity topLevel is
```

```
    port (SEL, A, B: in STD_LOGIC;
```

```
          F : out STD_LOGIC);
```

```
end entity;
```

```
architecture STRUCTURE of topLevel is
```

```
    component INVERTER
```

```
        port (A: in STD_LOGIC;
```

```
              F: out STD_LOGIC);
```

```
    end component;
```

```
    component AOI
```

```
        port (A, B, C, D: in STD_LOGIC;
```

```
              F : out STD_LOGIC);
```

```
    end component;
```

```
    signal SELB: STD_LOGIC;
```

```
begin
```


```
    G1: INVERTER port map (SEL, SELB);
```

```
    G2: AOI port map (SEL, A, SELB, B, F);
```

```
end architecture;
```

Port Maps

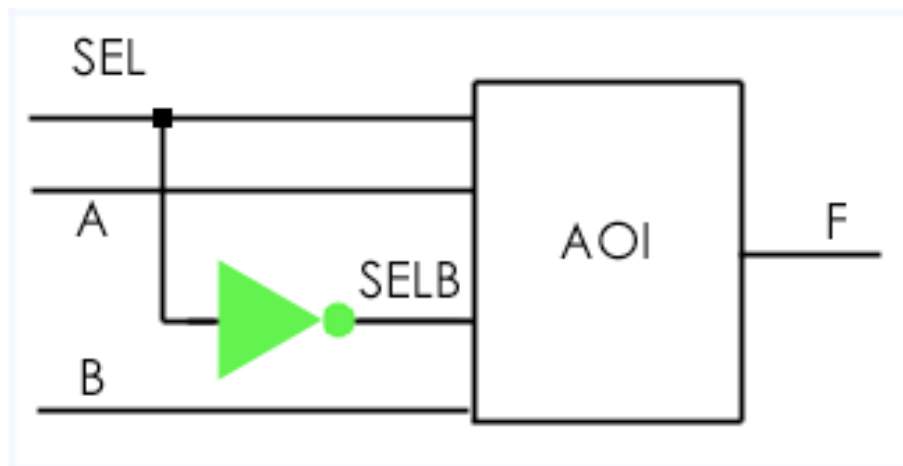- The ports in a component declaration must usually match the ports in the entity declaration one-for-one.
- The component declaration defines the names, order, mode and types of the ports to be used when the component is instanced in the architecture body.



```
--topLevel.vhd
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

```
entity topLevel is
```

```
    port (SEL, A, B: in STD_LOGIC;
```

```
          F : out STD_LOGIC);
```

```
end entity;
```

```
architecture STRUCTURE of topLevel is
```

```
    component INVERTER
```

```
        port (A: in STD_LOGIC;
```

```
              F: out STD_LOGIC);
```

```
    end component;
```

```
    component AOI
```

```
        port (A, B, C, D: in STD_LOGIC;
```

```
              F : out STD_LOGIC);
```

```
    end component;
```

```
    signal SELB: STD_LOGIC;
```

```
begin
```


```
    G1: INVERTER port map (SEL, SELB);
```

```
    G2: AOI port map (SEL, A, SELB, B, F);
```

```
end architecture;
```

Port Maps

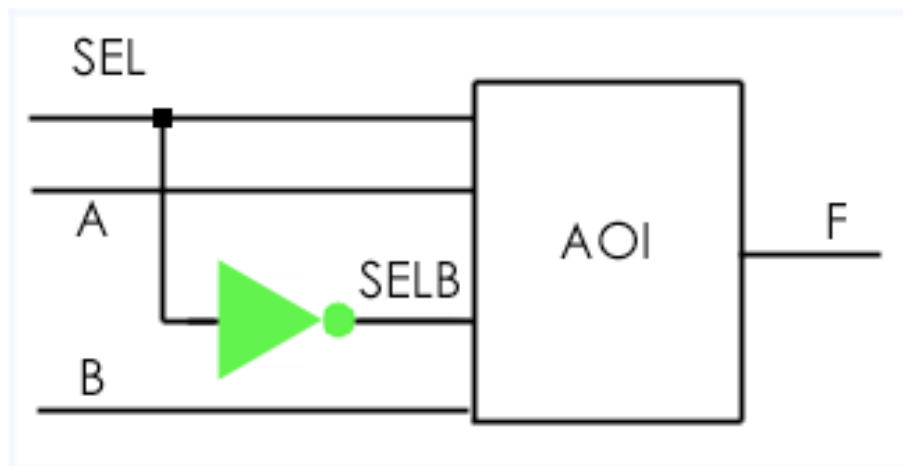- Instantiating a component implies making a local copy of the corresponding design entity
- A component is declared once within any architecture, but may be instanced any number of times.
- In this example, there is just one instance of the components **AOI** and **INVERTER**.



```
--topLevel.vhd
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

```
entity topLevel is
```

```
    port (SEL, A, B: in STD_LOGIC;
```

```
          F : out STD_LOGIC);
```

```
end entity;
```

```
architecture STRUCTURE of topLevel is
```

```
    component INVERTER
```

```
        port (A: in STD_LOGIC;
```

```
              F: out STD_LOGIC);
```

```
    end component;
```

```
    component AOI
```

```
        port (A, B, C, D: in STD_LOGIC;
```

```
              F : out STD_LOGIC);
```

```
    end component;
```

```
    signal SELB: STD_LOGIC;
```

```
begin
```


```
    G1: INVERTER port map (SEL, SELB);
```

```
    G2: AOI port map (SEL, A, SELB, B, F);
```

```
end architecture;
```

Association

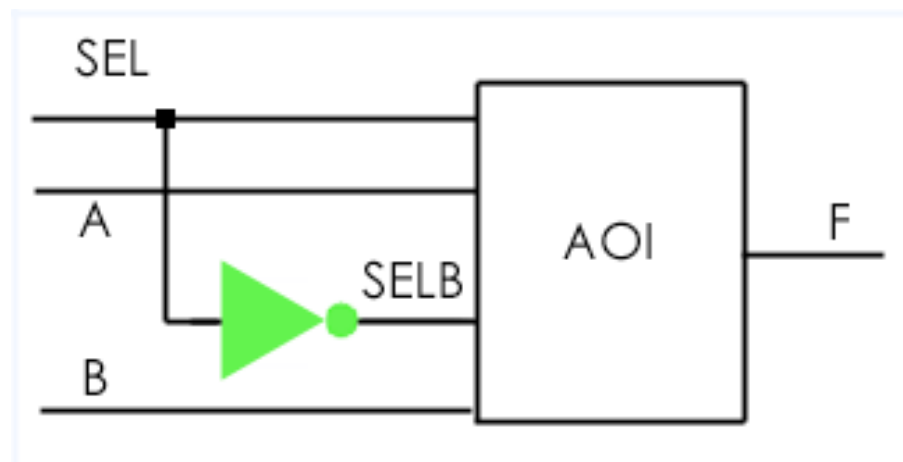- Signals in an architecture are associated with ports on a component using a port map.
- A port map makes a connection between “pieces of wire” (signals) and pins on a component (ports).
- Signal SELB is associated with the F port of the INV instance and the C port of the AOI instance.



```
--topLevel.vhd
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;
```

```
entity topLevel is  
    port (SEL, A, B: in STD_LOGIC;  
          F : out STD_LOGIC);  
end entity;
```

```
architecture STRUCTURE of topLevel is
```

```
    component INVERTER  
        port (A: in STD_LOGIC;  
              F: out STD_LOGIC);  
    end component;
```

```
    component AOI  
        port (A, B, C, D: in STD_LOGIC;  
              F : out STD_LOGIC);  
    end component;
```

```
    signal SELB: STD_LOGIC;
```

```
begin
```

```
    G1: INVERTER port map (SEL, SELB);
```




```
    G2: AOI port map (SEL, A, SELB, B, F);
```

```
end architecture;
```



Printed Circuit Board (PCB) representation of components

Sockets and Chips



Sockets

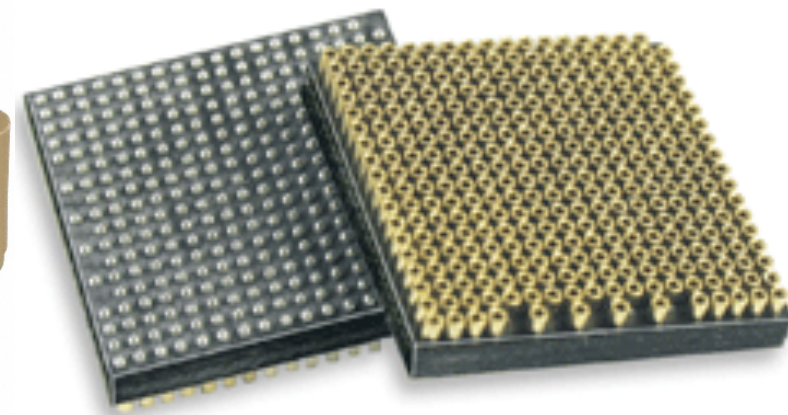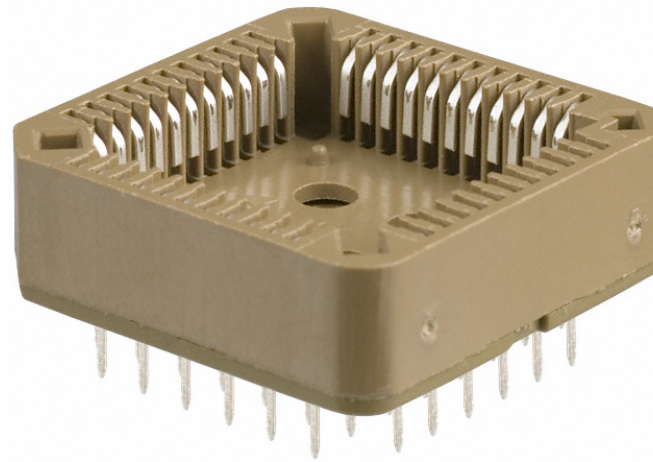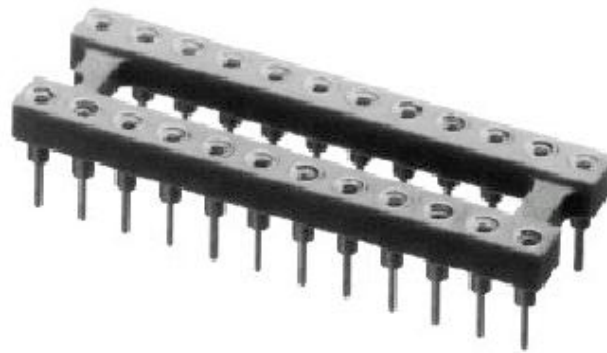

Chips

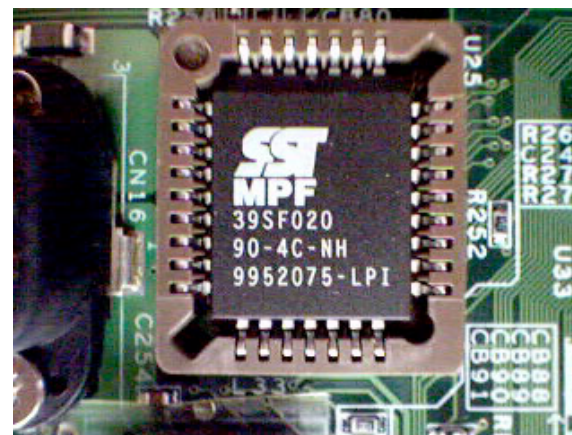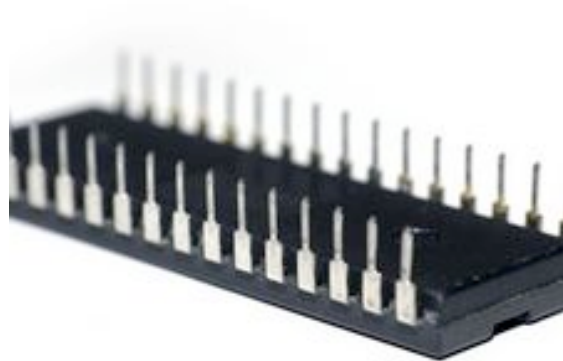

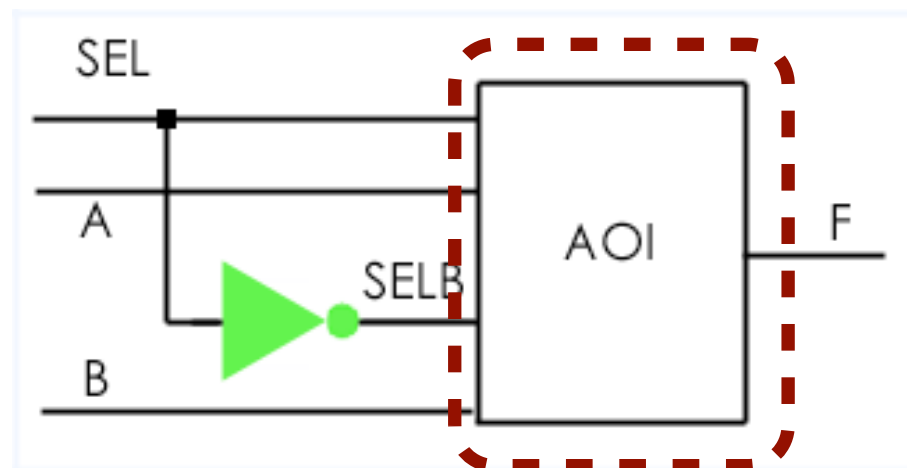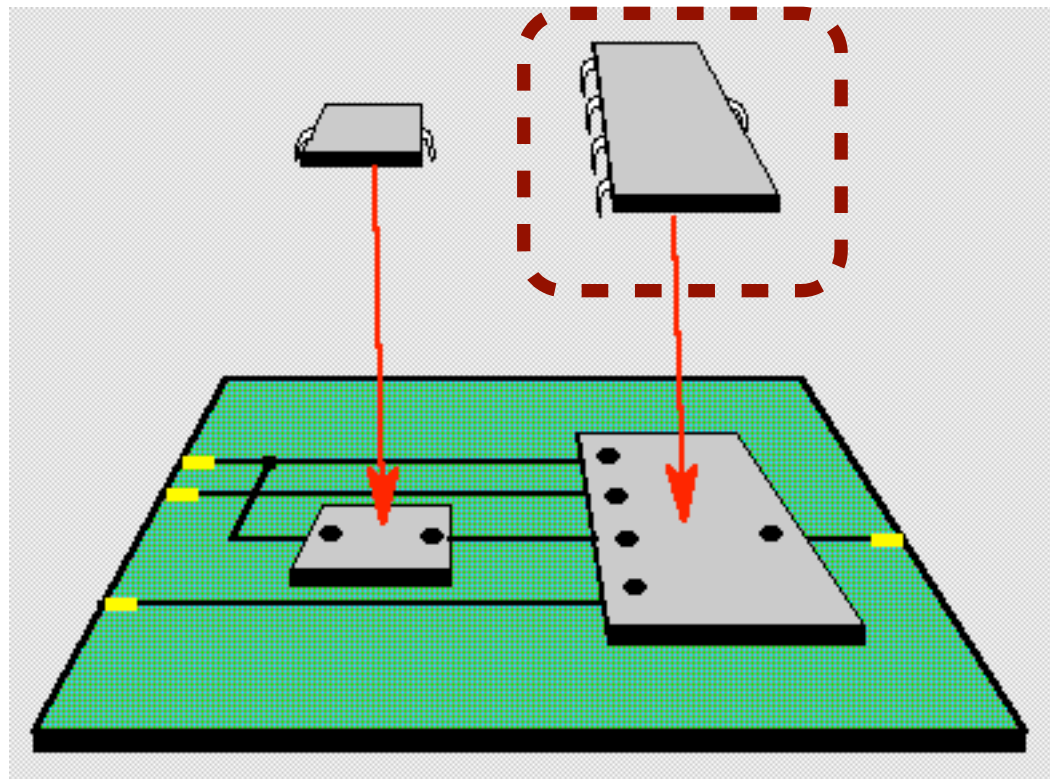
Components declaration are the list of chips we will use in our PCB



- Instantiating components in VHDL enables us to create a design hierarchy
- It's just like plugging chips into a PCB.
- In our case, the **topLevel** is the PCB, the AOI gate and INVERTER gate are two chips.

```
--this is a component declaration
component AOI
  port (A, B, C, D: in STD_LOGIC;
        F : out STD_LOGIC);
end component;
```

Component instances are the sockets



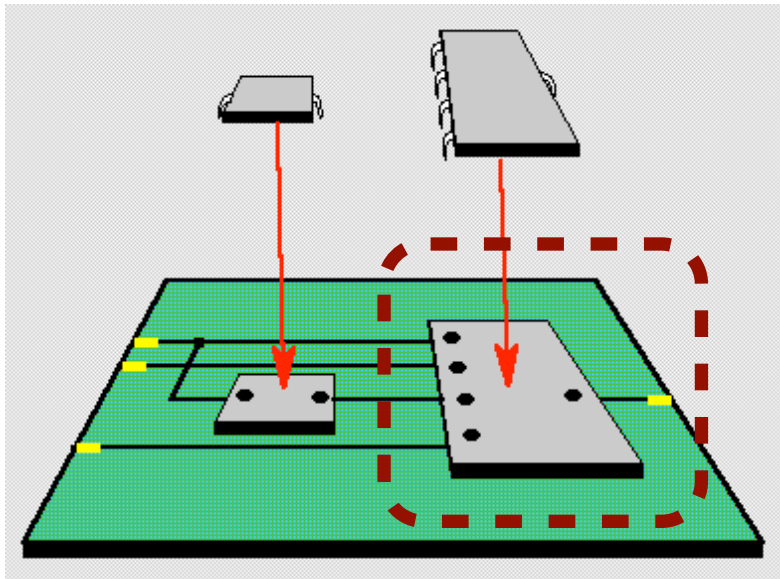


```
--this is a component declaration
component AOI
  port (A, B, C, D: in STD_LOGIC;
        F : out STD_LOGIC);
end component;
```

(...)

```
--this is a component instantiation
G2: AOI port map (SEL, A, SELB, B, F);
```

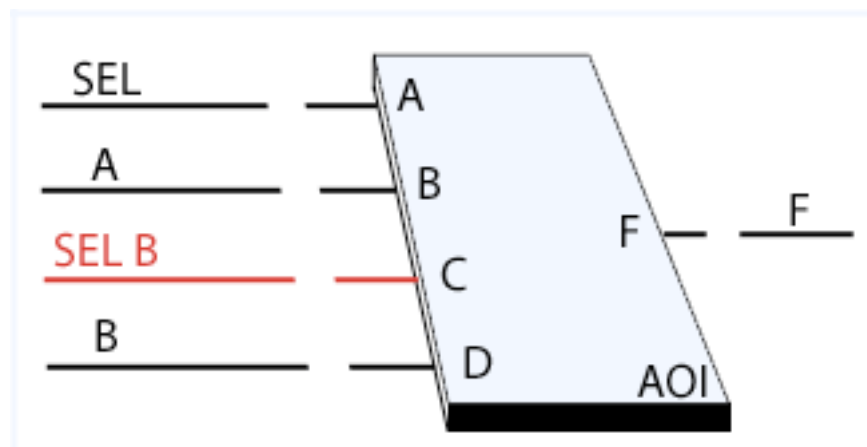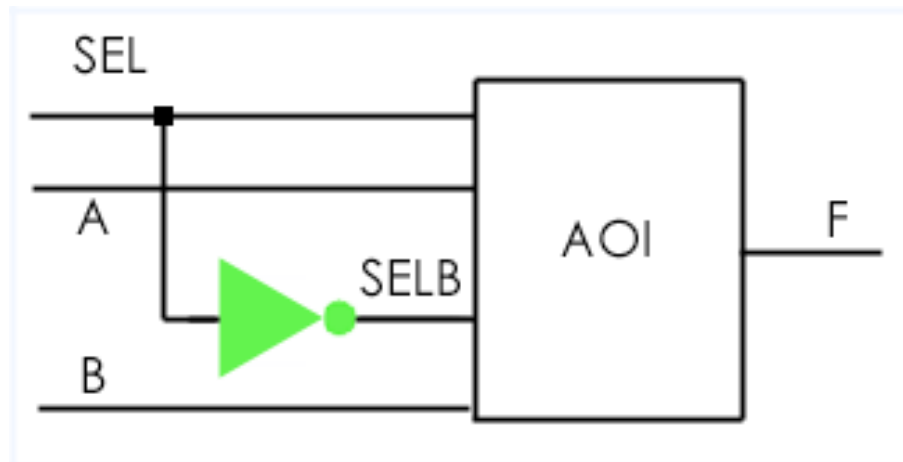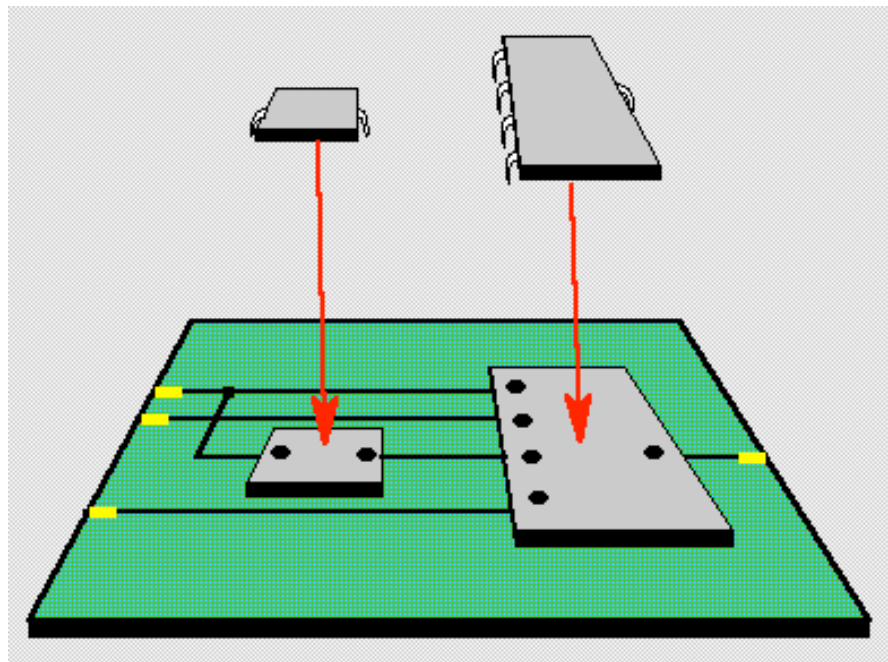- Instantiation is essentially a VHDL term for soldering a chip socket into a PCB.
- Instantiation also assumes that the socket contains the chip referenced by the same name as it is plugged into the PCB.



```
--topLevel.vhd
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

```
entity topLevel is
```

```
    port (SEL, A, B: in STD_LOGIC;
```

```
          F : out STD_LOGIC);
```

```
end entity;
```

```
architecture STRUCTURE of topLevel is
```

```
    component INVERTER
```

```
        port (A: in STD_LOGIC;
```

```
              F: out STD_LOGIC);
```

```
    end component;
```

```
    component AOI
```

```
        port (A, B, C, D: in STD_LOGIC;
```

```
              F : out STD_LOGIC);
```

```
    end component;
```

```
    signal SELB: STD_LOGIC;
```

```
begin
```

```
    G1: INVERTER port map (SEL, SELB);
```

```
    G2: AOI port map (SEL, A, SELB, B, F);
```

```
end architecture;
```

Summary of a component declaration

COMPONENT declaration:

```
COMPONENT component_name IS
  PORT (
    port_name : signal_mode signal_type;
    port_name : signal_mode signal_type;
    ...);
END COMPONENT;
```

```
--this is a component declaration
component AOI
  port (A, B, C, D: in STD_LOGIC;
        F : out STD_LOGIC);
end component;
```

The names of the ports must be specified, along with their modes (IN, OUT, BUFFER, or INOUT) and data types (STD_LOGIC_VECTOR, INTEGER, BOOLEAN, etc.)


Summary of a component instantiation

COMPONENT instantiation:

```
label: component_name PORT MAP (port_list);
```


```
--this is a component instantiation  
G2: AOI port map (SEL, A, SELB, B, F);
```

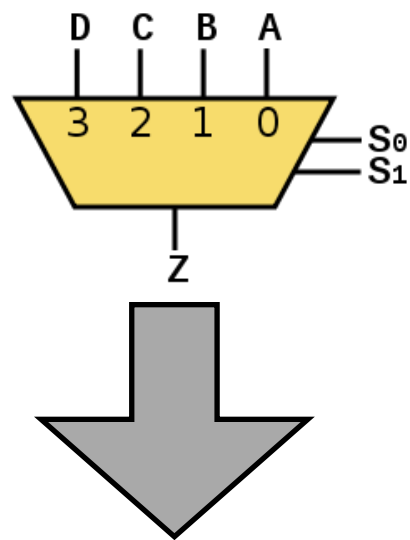**A test-bench is just a PCB that
tests your component!**



```
entity mux is
    port(a,b,c,d,s0,s1 : in bit;
          z : out bit);
end entity;

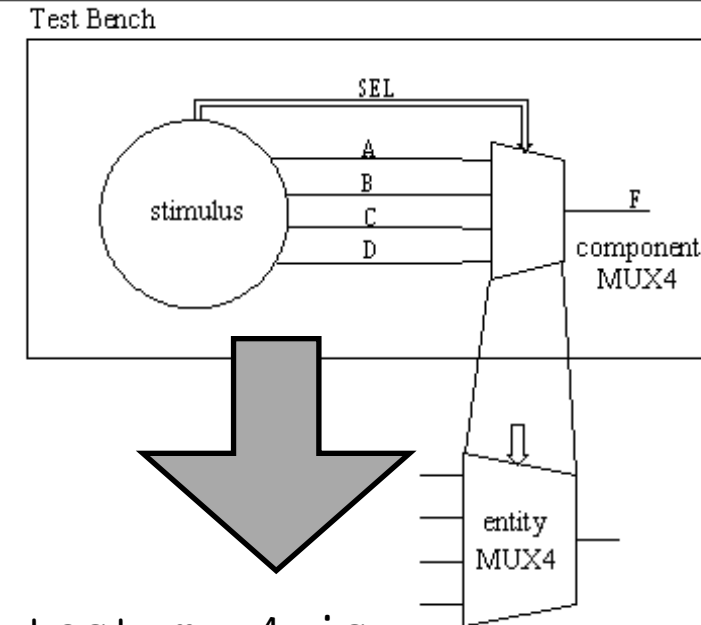architecture myarch of mux is
begin
    z <=
        (a AND NOT(s0) AND NOT(s1))
    OR
        (b AND s0 AND NOT(s1))
    OR
        (c AND NOT(s0) AND s1)
    OR
        (d AND s0 AND s1);
end architecture ;
```



```
entity test_mux4 is
end;

architecture bench of test_mux4 is
    component mux
        port (a, b, c, d, s0, s1: in bit;
              z :out bit);
    end component;

    signal a, b, c, d, z, s0, s1: bit;


begin
    s0 <= '0', '1' after 20 ns;
    s1 <= '0', '1' after 10ns;
    a  <= '0', '1' after 5 ns;
    b  <= '0', '1' after 20 ns, '0' after 30 ns;
    c  <= '0', '1' after 10 ns, '0' after 20 ns;
    d  <= '0', '1' after 15 ns, '1' after 25 ns;

    m: mux port map (a, b, c, d, s0, s1, z);

end bench;
```

More complex example: ALU made of components

General Structure

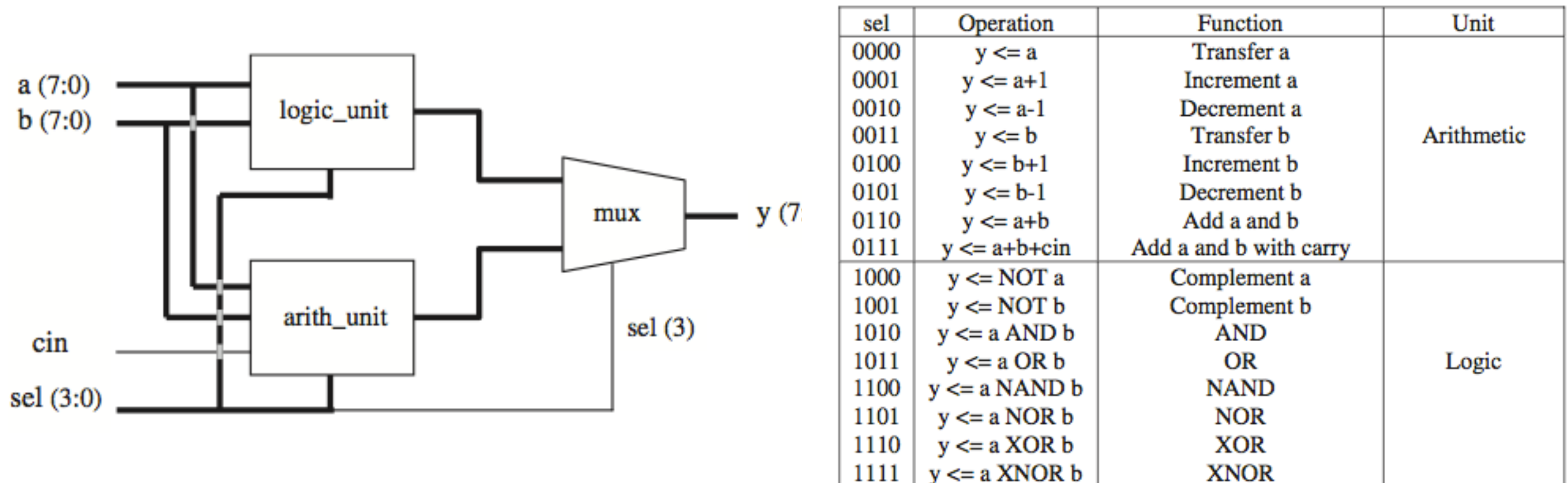


This design will have 4 different files: One for each component description (logic_unit, arithm_unit and MUX) and a single file for the top level.

arith_unit

```

1  ----- COMPONENT arith_unit: -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  USE ieee.std_logic_unsigned.all;
5  -----
6  ENTITY arith_unit IS
7      PORT ( a, b: IN STD_LOGIC_VECTOR (7 DOWNT0 0);
8            sel: IN STD_LOGIC_VECTOR (2 DOWNT0 0);
9            cin: IN STD_LOGIC;
10           x: OUT STD_LOGIC_VECTOR (7 DOWNT0 0));
11 END arith_unit;
12 -----
13 ARCHITECTURE arith_unit OF arith_unit IS
14     SIGNAL arith, logic: STD_LOGIC_VECTOR (7 DOWNT0 0);
15 BEGIN
16     WITH sel SELECT
17         x <=  a WHEN "000",
18             a+1 WHEN "001",
19             a-1 WHEN "010",
20             b WHEN "011",
21             b+1 WHEN "100",
22             b-1 WHEN "101",
23             a+b WHEN "110",
24             a+b+cin WHEN OTHERS;
25 END arith_unit;
26 -----

```

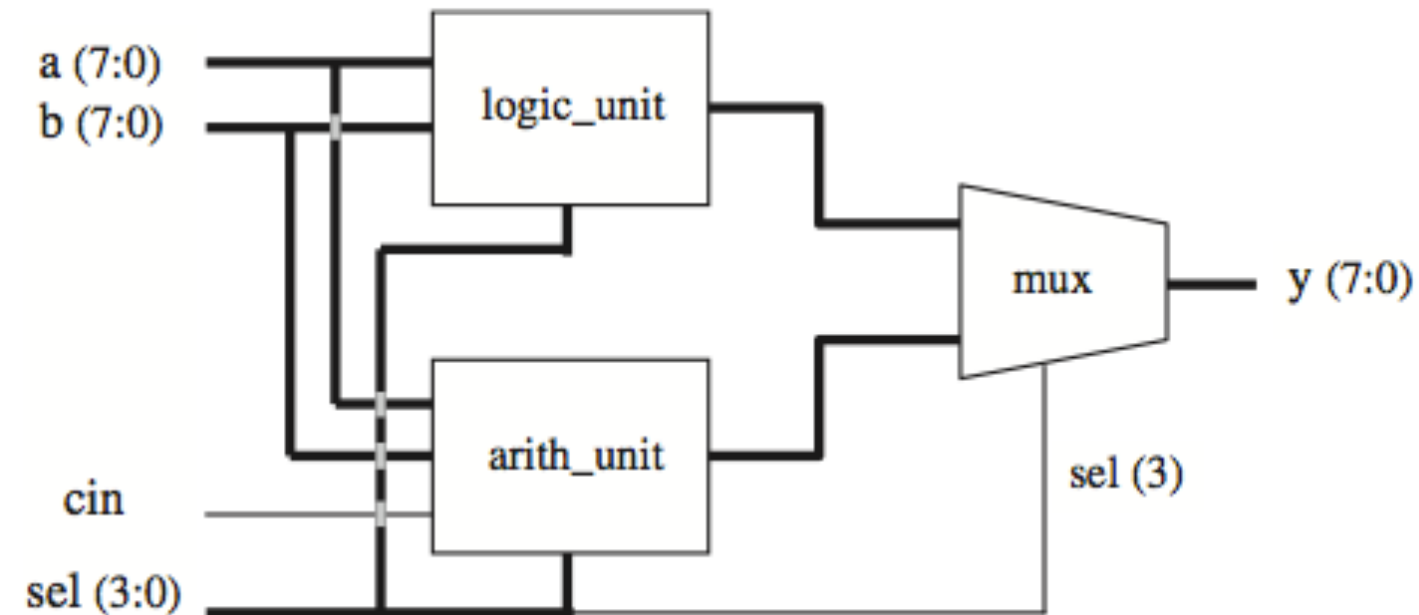


sel	Operation	Function	Unit
0000	y <= a	Transfer a	Arithmetic
0001	y <= a+1	Increment a	
0010	y <= a-1	Decrement a	
0011	y <= b	Transfer b	
0100	y <= b+1	Increment b	
0101	y <= b-1	Decrement b	
0110	y <= a+b	Add a and b	
0111	y <= a+b+cin	Add a and b with carry	
1000	y <= NOT a	Complement a	Logic
1001	y <= NOT b	Complement b	
1010	y <= a AND b	AND	
1011	y <= a OR b	OR	
1100	y <= a NAND b	NAND	
1101	y <= a NOR b	NOR	
1110	y <= a XOR b	XOR	
1111	y <= a XNOR b	XNOR	

logic_unit

```

1  ----- COMPONENT logic_unit: -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  ENTITY logic_unit IS
6      PORT ( a, b: IN STD_LOGIC_VECTOR (7 DOWNT0 0);
7            sel: IN STD_LOGIC_VECTOR (2 DOWNT0 0);
8            x: OUT STD_LOGIC_VECTOR (7 DOWNT0 0));
9  END logic_unit;
10 -----
11 ARCHITECTURE logic_unit OF logic_unit IS
12 BEGIN
13     WITH sel SELECT
14         x <= NOT a WHEN "000",
15             NOT b WHEN "001",
16             a AND b WHEN "010",
17             a OR b WHEN "011",
18             a NAND b WHEN "100",
19             a NOR b WHEN "101",
20             a XOR b WHEN "110",
21             NOT (a XOR b) WHEN OTHERS;
22 END logic_unit;
23 -----

```

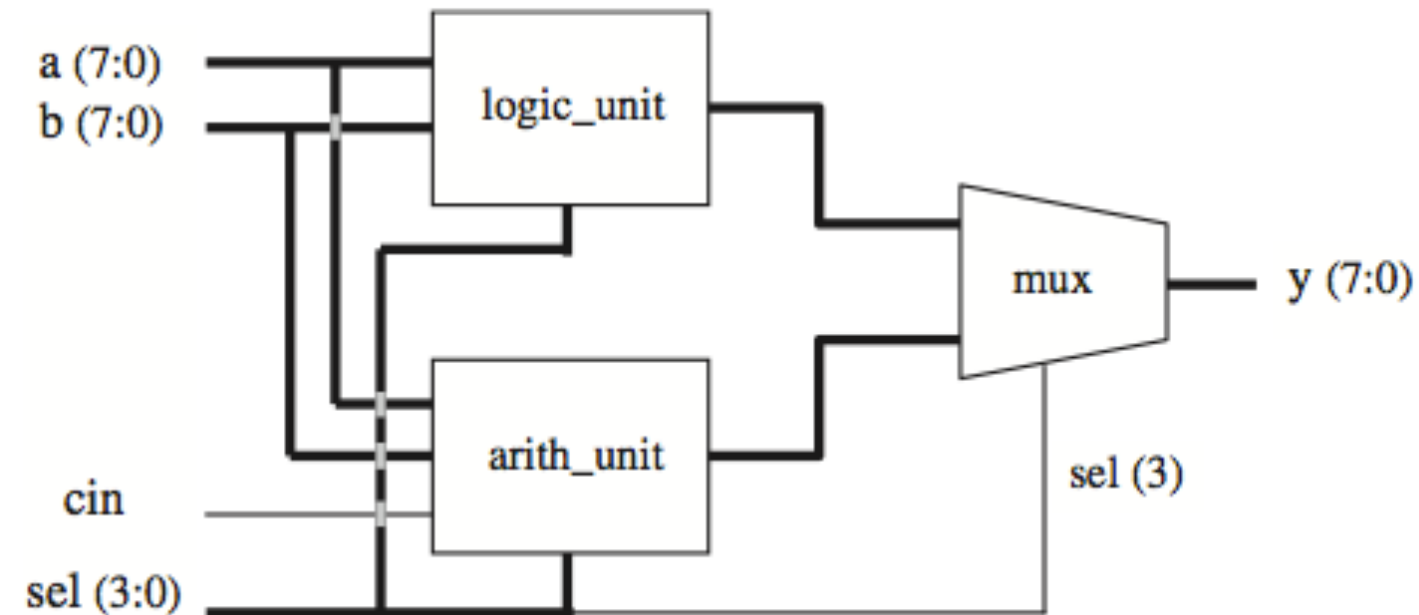


sel	Operation	Function	Unit
0000	y <= a	Transfer a	Arithmetic
0001	y <= a+1	Increment a	
0010	y <= a-1	Decrement a	
0011	y <= b	Transfer b	
0100	y <= b+1	Increment b	
0101	y <= b-1	Decrement b	
0110	y <= a+b	Add a and b	
0111	y <= a+b+cin	Add a and b with carry	
1000	y <= NOT a	Complement a	Logic
1001	y <= NOT b	Complement b	
1010	y <= a AND b	AND	
1011	y <= a OR b	OR	
1100	y <= a NAND b	NAND	
1101	y <= a NOR b	NOR	
1110	y <= a XOR b	XOR	
1111	y <= a XNOR b	XNOR	

mux

```

1  ----- COMPONENT mux: -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  ENTITY mux IS
6      PORT ( a, b: IN STD_LOGIC_VECTOR (7 DOWNT0 0);
7            sel: IN STD_LOGIC;
8            x: OUT STD_LOGIC_VECTOR (7 DOWNT0 0));
9  END mux;
10 -----
11 ARCHITECTURE mux OF mux IS
12 BEGIN
13     WITH sel SELECT
14         x <=  a WHEN '0',
15              b WHEN OTHERS;
16 END mux;
17 -----

```

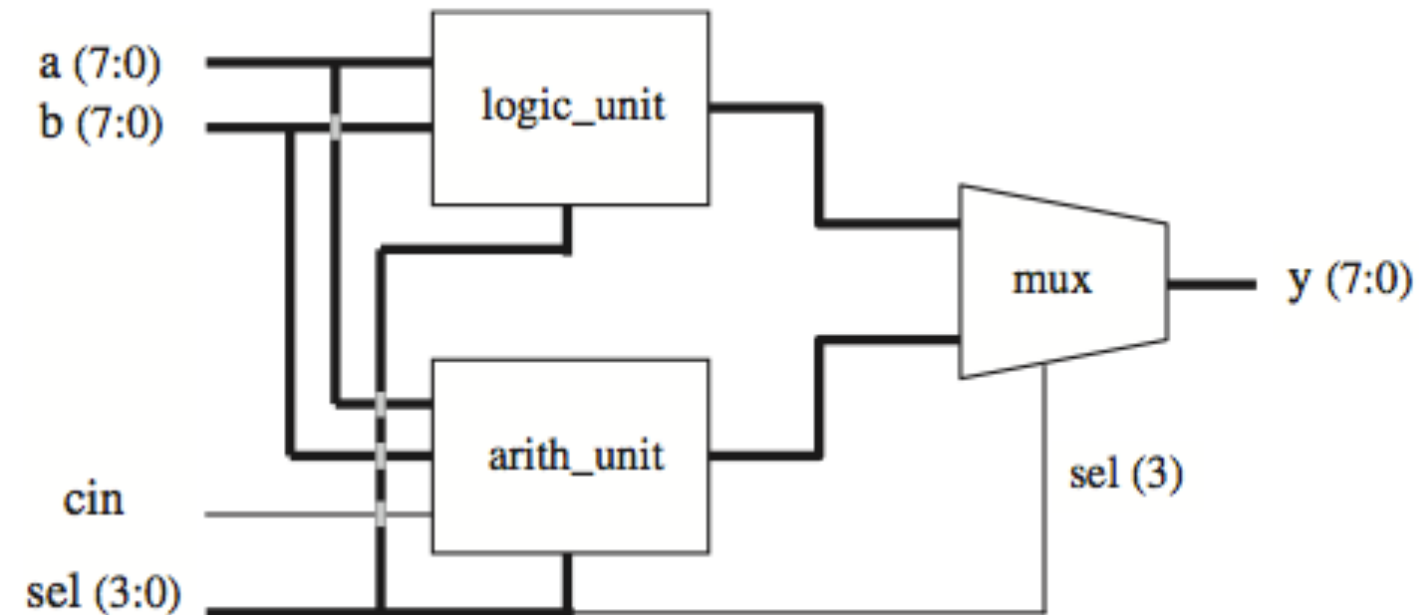


sel	Operation	Function	Unit
0000	y <= a	Transfer a	Arithmetic
0001	y <= a+1	Increment a	
0010	y <= a-1	Decrement a	
0011	y <= b	Transfer b	
0100	y <= b+1	Increment b	
0101	y <= b-1	Decrement b	
0110	y <= a+b	Add a and b	
0111	y <= a+b+cin	Add a and b with carry	
1000	y <= NOT a	Complement a	Logic
1001	y <= NOT b	Complement b	
1010	y <= a AND b	AND	
1011	y <= a OR b	OR	
1100	y <= a NAND b	NAND	
1101	y <= a NOR b	NOR	
1110	y <= a XOR b	XOR	
1111	y <= a XNOR b	XNOR	

```

1  ----- Project ALU (main code): -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  ENTITY alu IS
6      PORT ( a, b: IN STD_LOGIC_VECTOR(7 DOWNTO 0);
7            cin: IN STD_LOGIC;
8            sel: IN STD_LOGIC_VECTOR(3 DOWNTO 0);
9            v: OUT STD LOGIC VECTOR(7 DOWNTO 0));
10 END alu;
11 -----
12 ARCHITECTURE alu OF alu IS
13 -----
14     COMPONENT arith_unit IS
15     PORT ( a, b: IN STD_LOGIC_VECTOR(7 DOWNTO 0);
16           cin: IN STD_LOGIC;
17           sel: IN STD_LOGIC_VECTOR(2 DOWNTO 0);
18           x: OUT STD_LOGIC_VECTOR(7 DOWNTO 0));
19     END COMPONENT;
20 -----
21     COMPONENT logic_unit IS
22     PORT ( a, b: IN STD_LOGIC_VECTOR(7 DOWNTO 0);
23           sel: IN STD_LOGIC_VECTOR(2 DOWNTO 0);
24           x: OUT STD_LOGIC_VECTOR(7 DOWNTO 0));
25     END COMPONENT;
26 -----
27     COMPONENT mux IS
28     PORT ( a, b: IN STD_LOGIC_VECTOR(7 DOWNTO 0);
29           sel: IN STD_LOGIC;
30           x: OUT STD_LOGIC_VECTOR(7 DOWNTO 0));
31     END COMPONENT;
32 -----
33     SIGNAL x1, x2: STD_LOGIC_VECTOR(7 DOWNTO 0);
34 -----
35 BEGIN
36     U1: arith_unit PORT MAP (a, b, cin, sel(2 DOWNTO 0), x1);
37     U2: logic_unit PORT MAP (a, b, sel(2 DOWNTO 0), x2);
38     U3: mux PORT MAP (x1, x2, sel(3), y);
39 END alu;
40 -----

```

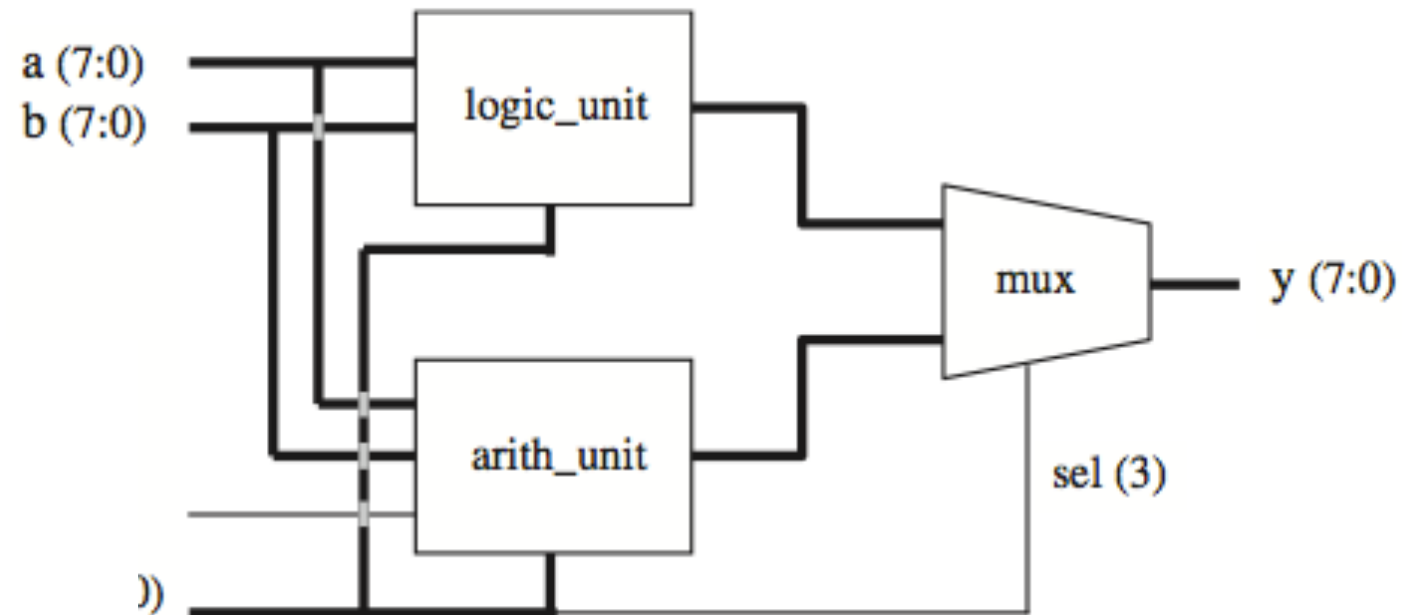

	Operation	Function	Unit
0	y <= a	Transfer a	Arithmetic
1	y <= a+1	Increment a	
0	y <= a-1	Decrement a	
1	y <= b	Transfer b	
0	y <= b+1	Increment b	
1	y <= b-1	Decrement b	
0	y <= a+b	Add a and b	
1	y <= a+b+cin	Add a and b with carry	
0	y <= NOT a	Complement a	Logic
1	y <= NOT b	Complement b	
0	y <= a AND b	AND	
1	y <= a OR b	OR	
0	y <= a NAND b	NAND	
1	y <= a NOR b	NOR	
0	y <= a XOR b	XOR	
1	y <= a XNOR b	XNOR	

main code

PORT MAP tricks

- There are two ways to map the PORTS of a COMPONENT during its instantiation: positional mapping and nominal mapping.

- Consider the following component declaration:

```
COMPONENT inverter IS  
    PORT (a: IN STD_LOGIC; b: OUT STD_LOGIC);  
END COMPONENT;  
...
```

- The following three instantiations are all identical.

```
U1 : inverter PORT MAP (x,y);  
U2 : inverter PORT MAP (y=>b,x=>a);  
U3 : inverter PORT MAP (x=>a,y=>b);
```

- Only in U1 the mapping is positional; that is, PORTS x and y correspond to a and b, respectively.

PORT MAP tricks

```
COMPONENT inverter IS
    PORT (a: IN STD_LOGIC; b: OUT STD_LOGIC);
END COMPONENT;
...
```

```
U1 : inverter PORT MAP (x,y);
U2 : inverter PORT MAP (y=>b,x=>a);
U3 : inverter PORT MAP (x=>a,y=>b);
```

- Positional mapping (U1) is easier to write.
- Nominal mapping (U2 and U3) is less error prone.

Ports can also be left unconnected (using the keyword OPEN). For example:

```
U2: my_circuit PORT MAP (x=>a, y=>b, w=>OPEN, z=>d);
```

Next time

- Next class we will talk about:
 - Packages
 - Generic Components